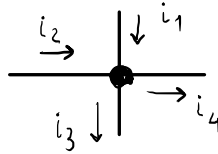


# LEYES de KIRCHOFF


• Ley de nodos:  $\sum_j i_j = 0$

↳ Cons de la carga




$$\Rightarrow \sum i_{\text{entrante}} = \sum i_{\text{saliente}}$$

• Ley de mallas

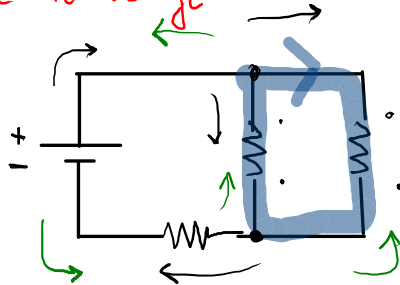

$$\sum \Delta V_{A,B} = 0$$

# AMPERÍMETRO y VOLTÍMETRO

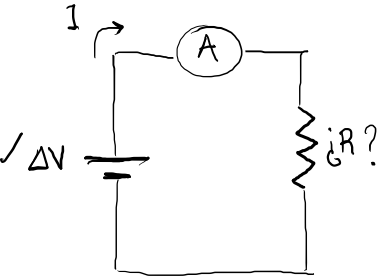


$$\Delta V = I_0 R$$

$$\frac{\Delta V}{I_0} = R$$

$$R_{TOT} = R + R_A$$

$$\frac{\Delta V}{R} \neq I' = \frac{\Delta V}{R + R_A}$$

$$R_A \ll R$$

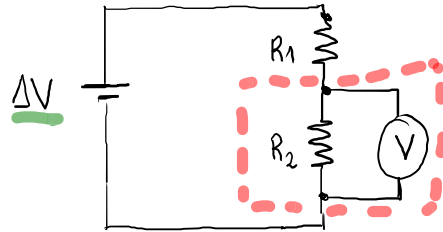

$$\Delta V_1 = R_1 I$$

$$\Delta V_2 = R_2 I$$

$$\Delta V = R_{TOT} I$$

$$R_{eq} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_V}} = \frac{R_2 R_V}{R_2 + R_V}$$

$$\approx R_2 : \text{ si } R_V \gg R_2$$

$$\Rightarrow R_2 + R_V \approx R_V$$

$$\Rightarrow R_{eq} \approx \frac{R_2 R_V}{R_V} = R_2$$

2.1.12)

$$I_1 = I_A = 500 \text{ mA} = 0,500 \text{ A}$$

a  $R_{eq}$  circuito

$$\begin{cases} R_1 = 2,00 \Omega \\ R_2 = 4 \text{ " " } \\ R_3 = 1 \text{ " " } \\ R_4 = 2 \text{ " " } \\ R_5 = 1 \text{ " " } \end{cases}$$

$$R_{eq_{45}} = \frac{R_4 R_5}{R_4 + R_5} = \frac{2}{3} \Omega = 0,667 \Omega$$

$$R_{eq_{345}} = R_3 + R_{eq_{45}} = \frac{5}{3} \Omega = 1,67 \Omega$$

$$R_{eq} = \frac{1}{\sum \frac{1}{R_i}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{345}}} = 0,741 \Omega$$

$$\{\Delta V = RI\}$$




b  $I_4$ ?


$$\begin{aligned} \Delta V_{xy} &= R_1 I_1 \\ &= (2,00 \Omega) \times (0,500 \text{ A}) \\ &= 1,00 \text{ V} \end{aligned}$$

$$\Rightarrow \Delta V_{xy} = I_3 R_{345}$$

$$\begin{aligned} \Rightarrow I_3 &= \frac{\Delta V_{xy}}{R_{345}} \\ &= 0,600 \text{ A} \end{aligned}$$
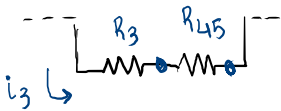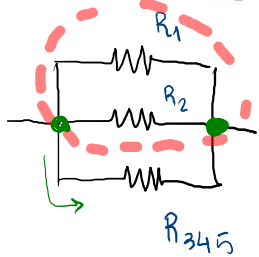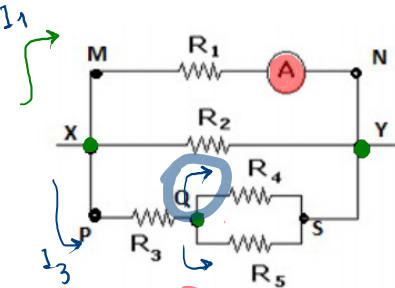
$$\begin{aligned} \Delta V_{QS} &= I_3 \cdot R_{45} \\ &= 0,400 \text{ V} \end{aligned}$$




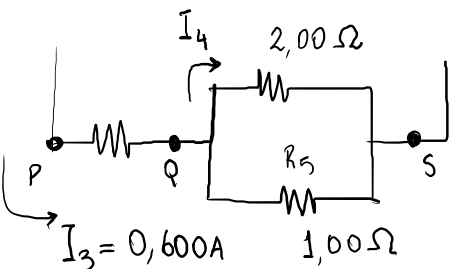


$$\Delta V_{QS} = 0,400\text{V} \Rightarrow I_4 = \frac{\Delta V_{QS}}{R_4} = 0,200\text{A}$$

$$I_5 = 0,400\text{A}$$

$$\Delta V_{PQ} = R_3 I_3 = 0,600\text{V}$$


|| d

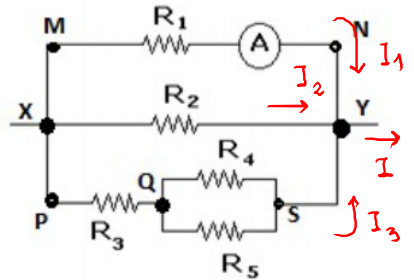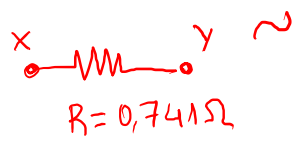

$I_{TOTAL}$   
 $I_1 + I_2 + I_3$

$$\left. \begin{aligned} R_{eq\ total} &= 0,741\ \Omega \\ \Delta V_{xy} &= 1,00\text{V} \end{aligned} \right\} I_T = 1,35\text{A}$$

# CIRCUITOS RC SERIE

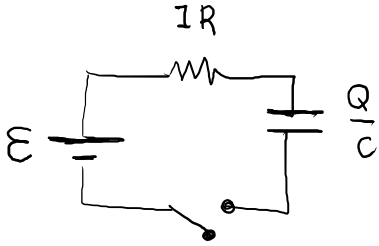



$$\Rightarrow \mathcal{E} = IR + \frac{Q}{C} \quad \frac{dQ}{dt} = I$$

$\tau = \text{cte de tiempo}$   
 $\tau = RC$

$$Q(t) = \underbrace{C\mathcal{E}}_{Q_0} (1 - e^{-t/\tau})$$


$$I(t) = \frac{\mathcal{E}}{R} e^{-t/\tau}$$

CARGA

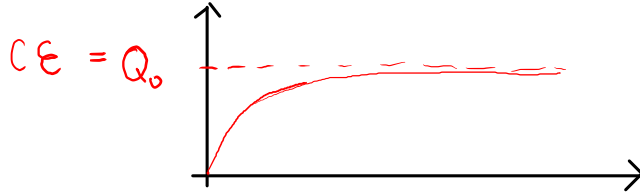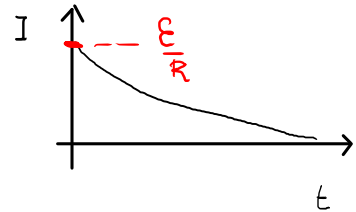

$x^0 = 1$   
 $e^{-\infty} \sim 0$

2.1.14

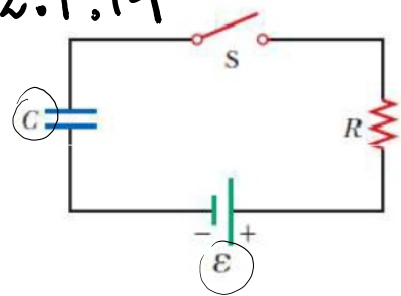

$R = 1,00 \text{ M}\Omega$ ,  $C = 5,00 \text{ }\mu\text{F}$  y  $\varepsilon = 30,0 \text{ V}$ .

$$\ln(e^x) = e^{\ln(x)} = x$$

a) ¿ $\tau$ ?  $\tau = RC = 5,00 \text{ s} = 1,00 \times 5,00 \times \underbrace{10^6 \times 10^{-6}}_1$

b) ¿ $Q_0$  = carga máxima?  $Q_0 = C\varepsilon = 0,150 \text{ mC} = 1,50 \times 10^{-4} \text{ C}$

c) ¿ $Q(10 \text{ s})$ ,  $I(10 \text{ s})$ ?

d)  $\Delta t$  para que  $Q = 75\%$  de  $Q_0 = \frac{3}{4} Q_0$

$\Leftrightarrow Q(t) = Q_0 [1 - e^{-t/\tau}] = \frac{3}{4} Q_0$

$$1 - e^{-t/\tau} = \frac{3}{4}$$

$$1 - \frac{3}{4} = \frac{1}{4} = e^{-t/\tau}$$



$$\ln\left(\frac{1}{4}\right) = \ln(e^{-t/\tau}) = -\frac{t}{\tau}$$

»

$$+1,39 = \frac{t}{\tau} \Rightarrow t = 1,39\tau$$

$t \approx 6,93 \text{ s}$

2.1.5

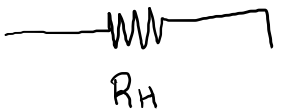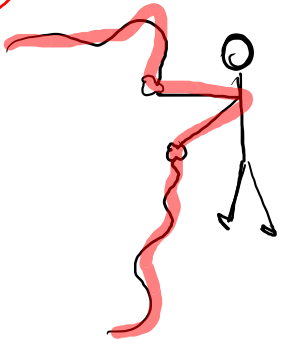


$$R_{\text{HUMANO}} = 1,0 \text{ k}\Omega$$

¿ $\Delta V$  xa que  $I = 10 \text{ mA}$ ?

$$\Delta V = R_H \cdot I = (1,0 \times 10^3) (10 \times 10^{-3}) = 10 \text{ V}$$

$$I = 100 \text{ mA} \rightarrow V = 100 \text{ V}$$

(2.2.1)

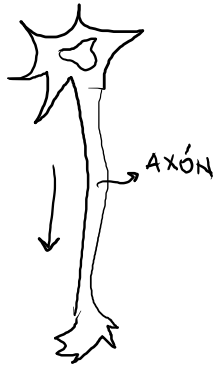

$$\rho = 2,0 \Omega \text{m} \leftarrow \text{axoplasma} \quad \rho_{\text{Cu}} = 1,72 \times 10^{-8} \Omega \text{m}$$

$$\underline{r = 5,0 \mu\text{m}} = 5,0 \times 10^{-6} \text{m} \rightarrow A = \pi r^2$$

$$L = 2,5 \text{ cm} = 0,025 \text{ m}$$

$$\text{¿R?} \quad R = \frac{\rho L}{A} = \frac{(2,0 \Omega \text{m}) \cdot (0,025 \text{ m})}{\pi \cdot (5,0 \times 10^{-6} \text{ m})^2} = 6,4 \times 10^8 \Omega \approx 640 \text{ M}\Omega$$


b

si  $r$  fuera más grande  $R \propto \frac{1}{r^2} \rightarrow R$  disminuye

$$\underline{c} \quad R = \frac{\rho_{\text{Cu}} L}{A} \rightarrow L = \frac{AR}{\rho_{\text{Cu}}} = 2900 \text{ km}$$



(2.2.2)

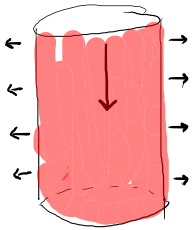

$R_o = \frac{\rho L}{A}$   
 $h = 2,5 \text{ cm}$


A = área membrana  
L = ancho membrana

$L = d$

$A = 2\pi r h$


resistencia de pérdida

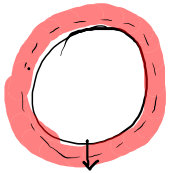$\Rightarrow R_o = \frac{R_m}{A} = \frac{R_m}{2\pi r h} = 2,55 \times 10^5 \Omega$



$R_m =$  resistencia metro cuadrado de membrana

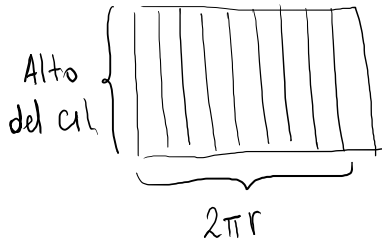$R_m = 0,20 \Omega \cdot m^2$   
 $2 \rho \cdot L$



$1 \text{ m}^2 \rightarrow R_m$

$\therefore A = 2\pi r h ?$

b con mielina  $R_m = 40 \Omega \cdot m^2$   
 $\Rightarrow R_o = 51 \text{ M}\Omega$