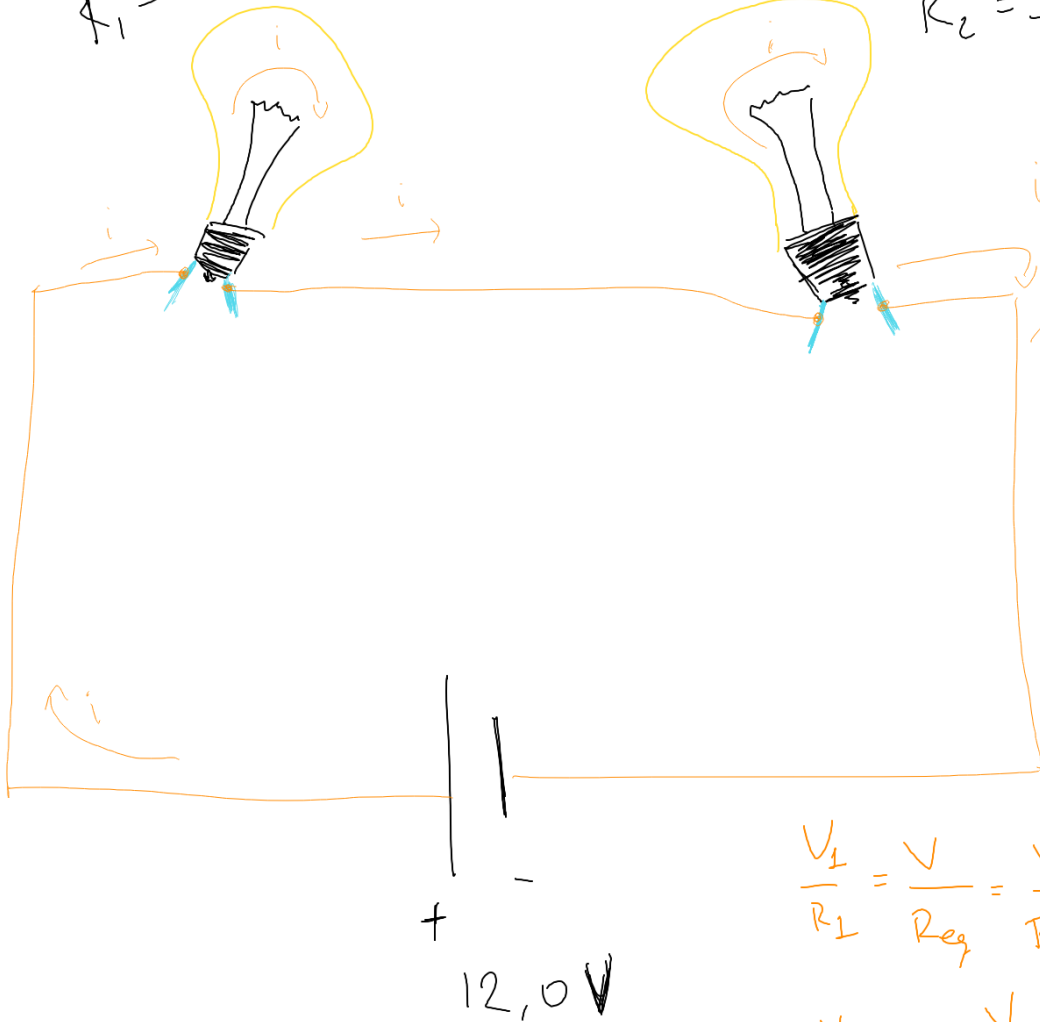


2.1.11)

$R_1 = 100 \Omega$

$R_2 = 50,0 \Omega$

$P = V_i = R i^2 = \frac{V^2}{R}$



en serie

$i = \frac{V}{R}$

$R_{eq} = R_1 + R_2$

$i_1 = i_2 = i_0$



$\frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V}{R_{eq}}$

$\frac{V_1}{R_1} = \frac{V}{R_{eq}} = \frac{V}{R_1 + R_2}$

$\frac{V_2}{R_2} = \frac{V}{R_1 + R_2}$



Interbdio:

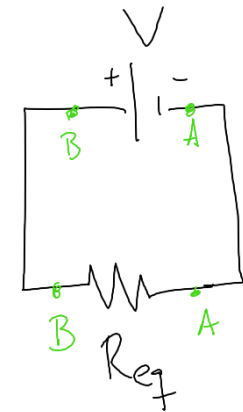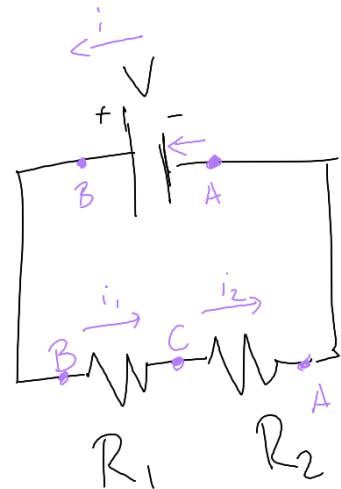

Lejes de Kirchhoff:

1) Nodos:  $\sum i_e = \sum i_s$  (en un nodo)

2) Mallas:  $\sum \Delta V = 0$  (en una malla)

$$\Delta V_{AB} = +V$$

$$\Delta V_{BC} = -i_1 R_1$$

$$\Delta V_{CA} = -i_2 R_2$$

$$\Delta V_{AB} = +V$$

$$\Delta V_{BA} = -i R_{eq}$$

2)  $\Delta V_{AB} + \Delta V_{BC} + \Delta V_{CA} = 0$  ( $i = i_1 = i_2$ )

$$V - i R_1 - i R_2 = 0 \Rightarrow V = i (R_1 + R_2)$$

$$\Delta V_{AB} + \Delta V_{BA} = 0$$



$$V - i R_{eq} = 0 \Rightarrow V = i R_{eq}$$

$$i (R_1 + R_2) = i R_{eq}$$

$$\Rightarrow R_{eq} = R_1 + R_2$$

Interlude 2.0)

$$V = \Delta V_1 = \Delta V_2$$

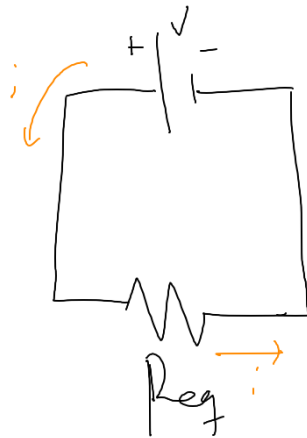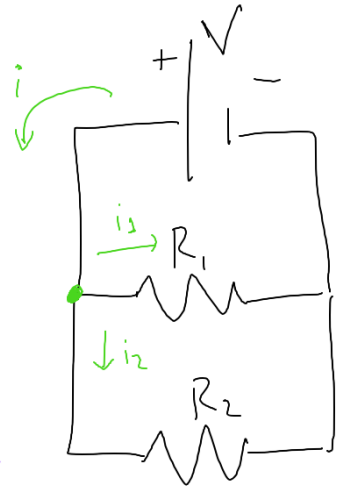

$$i = i_1 + i_2$$

$$V = i R_{eq} \rightarrow i = \frac{V}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2}$$

$$= \frac{R_1 + R_2}{R_1 R_2} = \frac{1}{R_{eq}}$$

$$\Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\Delta V_1 = R_1 i_1 \rightarrow i_1 = \frac{\Delta V_1}{R_1}$$



$$\Delta V_2 = R_2 i_2 \rightarrow i_2 = \frac{\Delta V_2}{R_2}$$

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}}$$


$$\frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2} = \frac{V}{R_{eq}}$$

$$V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = V \left( \frac{1}{R_{eq}} \right)$$

Interludio 3.0)

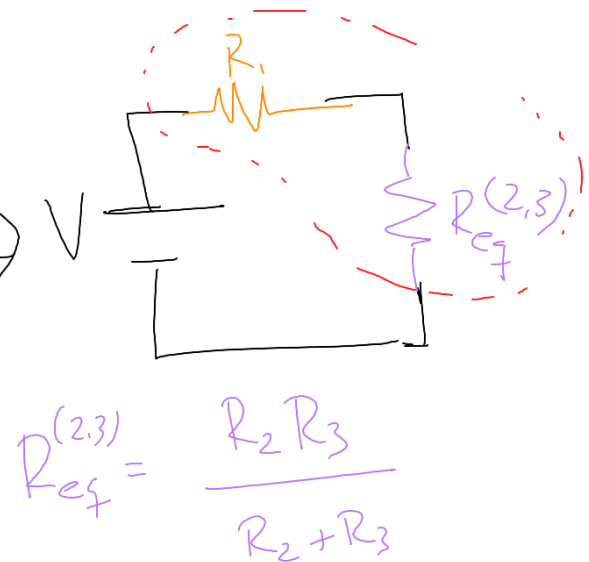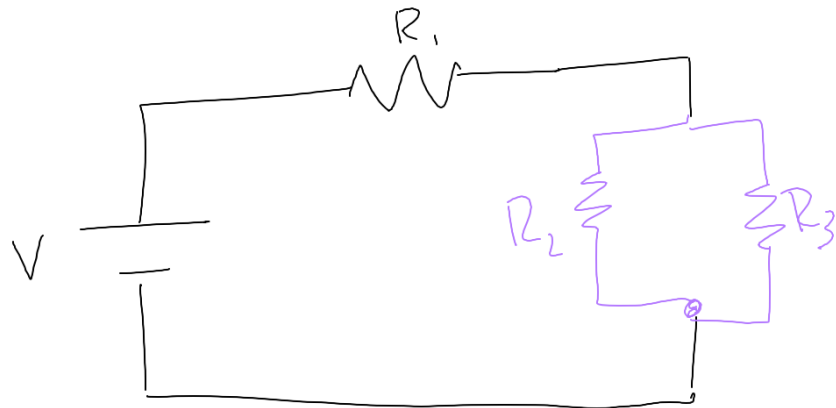
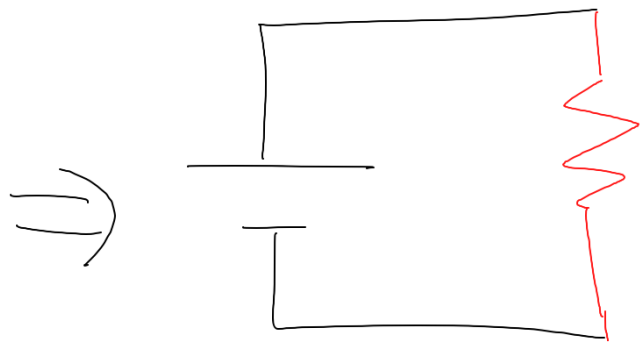
$$R_{eq}^{(2,3)} = \frac{R_2 R_3}{R_2 + R_3}$$




$$R_{eq} = R_1 + R_{eq}^{(2,3)} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

\*  $\frac{V_1}{R_1} = \frac{V}{R_1 + R_2} \Rightarrow V_1 = V \frac{R_1}{R_{eq}} \Rightarrow P_1 = \frac{V_1^2}{R_1} = \frac{V^2 R_1^2}{R_{eq}^2} \frac{1}{R_1}$

$$\Rightarrow P_1^{(s)} = \frac{V^2}{(R_1 + R_2)} R_1$$

$$V_1^2$$

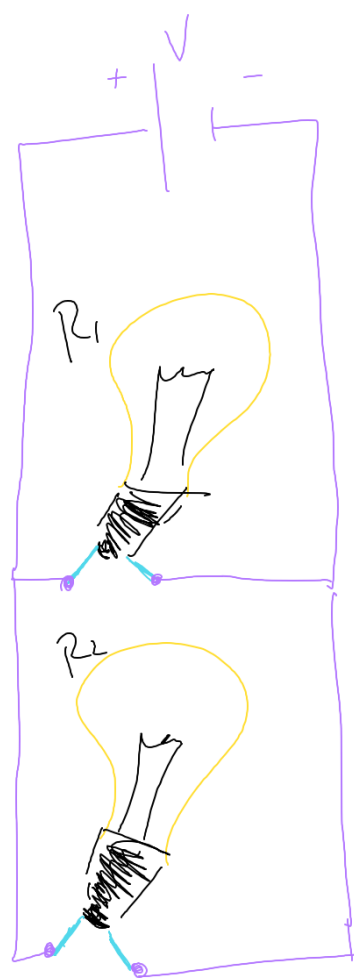


$$V = V_1 = V_2$$

$$P_1^{(P)} = \frac{V_1^2}{R_1} = \frac{V^2}{R_1}$$

$$\frac{P_1^{(P)}}{P_1^{(S)}} = \frac{\cancel{V^2} (R_1 + R_2)^2}{R_1 \cancel{V^2} R_1}$$

$$\frac{P_1^{(P)}}{P_1^{(S)}} = \frac{(R_1 + R_2)^2}{(R_1)^2} = \frac{(150 \Omega)^2}{(100 \Omega)^2} = 2,25$$

2.1.12)

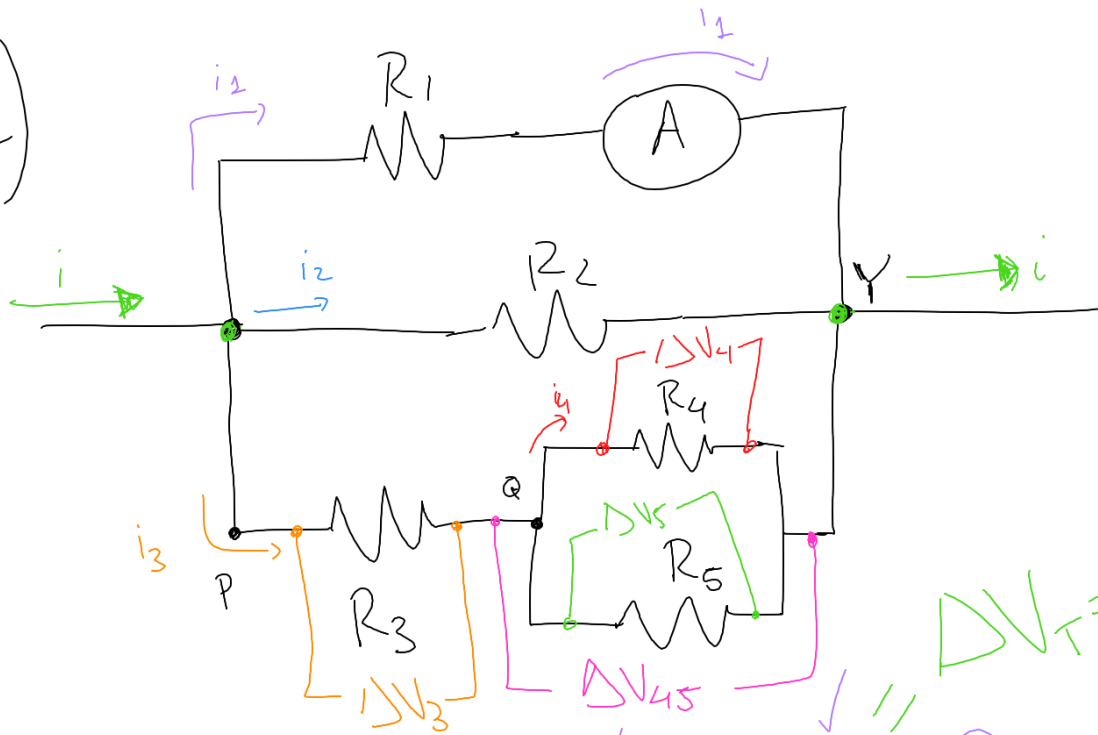

$$R_1 = 2,00 \Omega$$

$$R_2 = 4,00 \Omega$$

$$R_3 = 1,00 \Omega$$

$$R_4 = 2,00 \Omega$$

$$R_5 = 1,00 \Omega$$

$$i_1 = 500 \text{ mA}$$

2)

$$R_{45} = 0,667 \Omega$$

$$R_{345} = 1,66 \Omega$$

$$R_{eq} = 0,741 \Omega$$

b)

$$i_1 \rightarrow \Delta V_1 = R_1 i_1$$

$$\Delta V_2 = R_2 i_2 \rightarrow i_2 \checkmark$$

$$\Delta V_{345} = R_{345} i_3 \rightarrow i_3 \checkmark \rightarrow \Delta V_3 \checkmark \checkmark$$

$$\Delta V_T = R_{eq} i$$

$$\Delta V_{345} = \Delta V_3 + \Delta V_{45} \rightarrow \Delta V_{45} \checkmark$$

$$\parallel \checkmark \\ \Delta V_4 = R_4 i_4 \rightarrow i_4 \checkmark$$

$$\parallel \checkmark \\ \Delta V_5$$