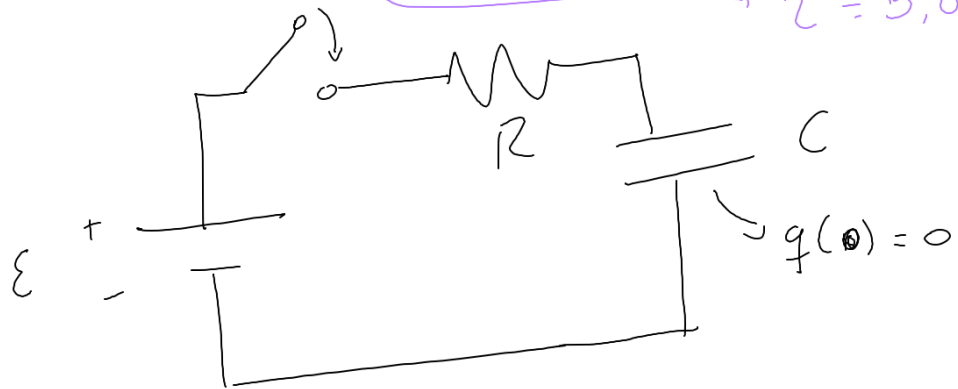


2.1.14) $C = 5,00 \times 10^{-6} \text{ F}$ $\epsilon = 30,0 \text{ V}$
 $R = 1,00 \times 10^6 \Omega$ $\tau = 5,00 \text{ s}$



Carga:

$$q(0) = 0$$

$$q(t) = C\epsilon \left(1 - e^{-t/RC}\right)$$


Annotations for the equation above:

- $C\epsilon$: Capacitancia
- ϵ : Fem de la batería
- $e^{-t/RC}$: Resistencia
- RC : Tiempo característico $\tau = RC (\Omega F)$

$$q(10) = \underbrace{C\epsilon}_{1,50 \times 10^{-4} \text{ C}} \left(1 - e^{-10/RC}\right)_{0.865} = 1,29 \times 10^{-4} \text{ C}$$

$$i(t) = \frac{\epsilon}{R} e^{-t/RC} = \frac{dq}{dt}$$
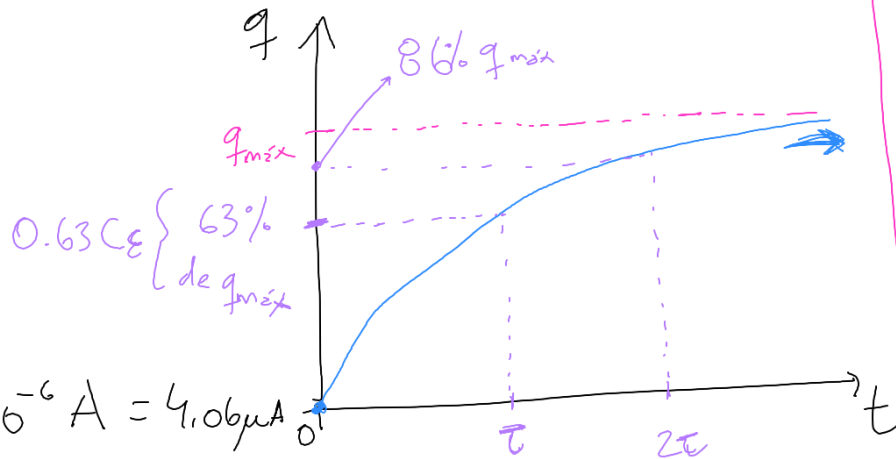
$$i(10) = \frac{\epsilon}{R} e^{-2} = \frac{\epsilon}{R} (0.135) = 4,06 \times 10^{-6} \text{ A} = 4,06 \mu\text{A}$$



En la práctica decimos que este "cargado" después de $t = 4 \sim 5 \tau$ (99,3%) (98,2%)

$$t^* / q(t^*) = 0.75 q_{\max}$$

$\log \neq \log_{10}$

$$q(t) = q_{\max} (1 - e^{-t/RC})$$

$$\Rightarrow 1 - e^{-t/RC} = 0.75$$

$$e^{-t/RC} = 0.25$$

$$\log(e^{-t/RC}) = \log(0.25)$$

$$-t/RC = \log(0.25)$$

$$t = \underbrace{-RC}_{5,005} \log(0.25) = 6.93 \text{ s}$$


2.1.6)

$$R_1 = 4 \text{ k}\Omega$$

$$R_2 = 7 \text{ k}\Omega$$

$$R_3 = 10 \text{ k}\Omega$$

$$R_4 = 9 \text{ k}\Omega$$

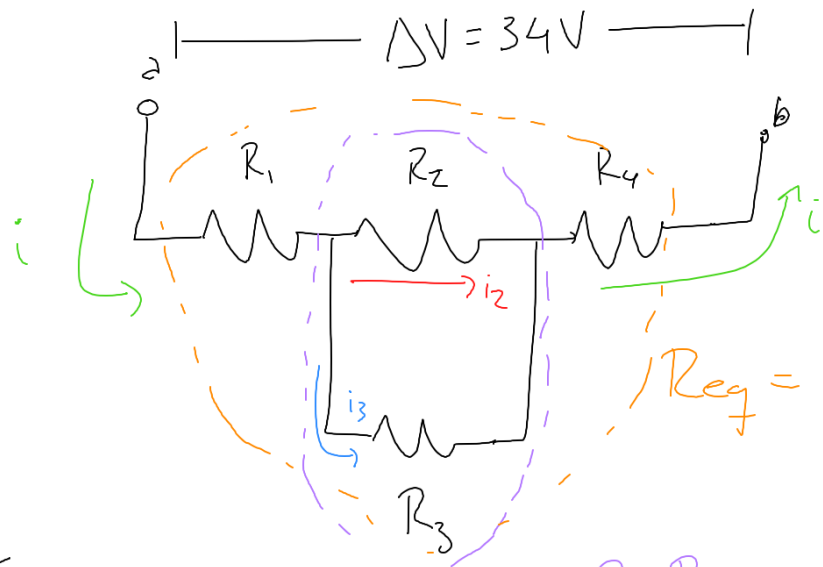

$$i = \frac{\Delta V}{R_{eq}} = 2 \times 10^{-3} \text{ A} = i_{R_2} = i_{R_4} \quad (2)$$

↓ 1 cifra

$$R_{eq} = R_1 + R_{23} + R_4 = 17 \text{ k}\Omega = 2 \times 10^1 \text{ k}\Omega$$

↓ 1 cifra

$$R_{23} = \frac{R_2 R_3}{R_2 + R_3} = 4,1 \text{ k}\Omega = 4 \text{ k}\Omega$$

↓ 1 cifra

$$P = \Delta V i = i^2 R$$


$$i_{R_{23}} = i = 2 \times 10^{-3} \text{ A}$$

$$\Delta V_{R_{23}} = R_{23} i_{R_{23}} = 8 \text{ V} = \Delta V_{R_2} = \Delta V_{R_3}$$

$$i_2 = \frac{\Delta V_{R_2}}{R_2} = 1 \times 10^{-3} \text{ A}$$

$$i_3 = \frac{\Delta V_{R_3}}{R_3} = 8 \times 10^{-4} \text{ A}$$

2.2.6)

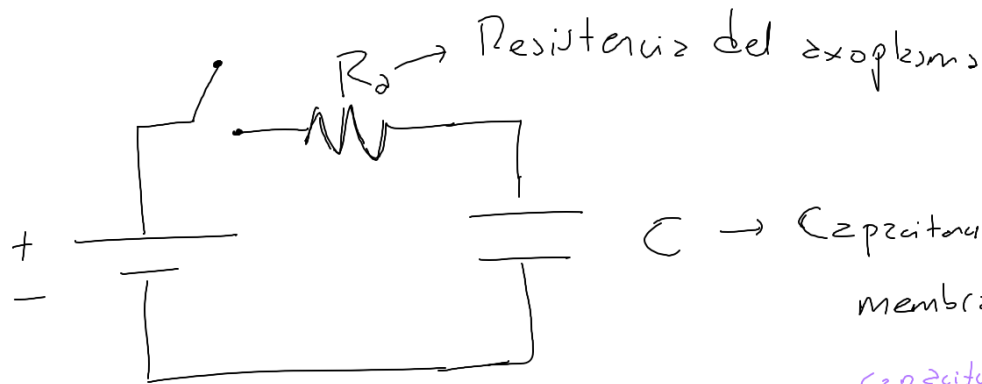

$$l = 2,5 \text{ cm} = 2,5 \times 10^{-2} \text{ m}$$

$$r_a = 5,0 \mu\text{m} = 5,0 \times 10^{-6} \text{ m}$$


$\tau = RC$

$$R_a = \frac{\rho_a l}{\pi r_a^2} = \frac{\rho L}{A} = 6,36 \times 10^8 \Omega$$

$$C = \frac{k_e \epsilon_0 A}{d} = \frac{k_e \epsilon_0 2\pi (r_a + d) l}{d} = 4,9 \times 10^{-9} \text{ F}$$

Capacitor de II

$$\tau = 3,1 \text{ s}$$

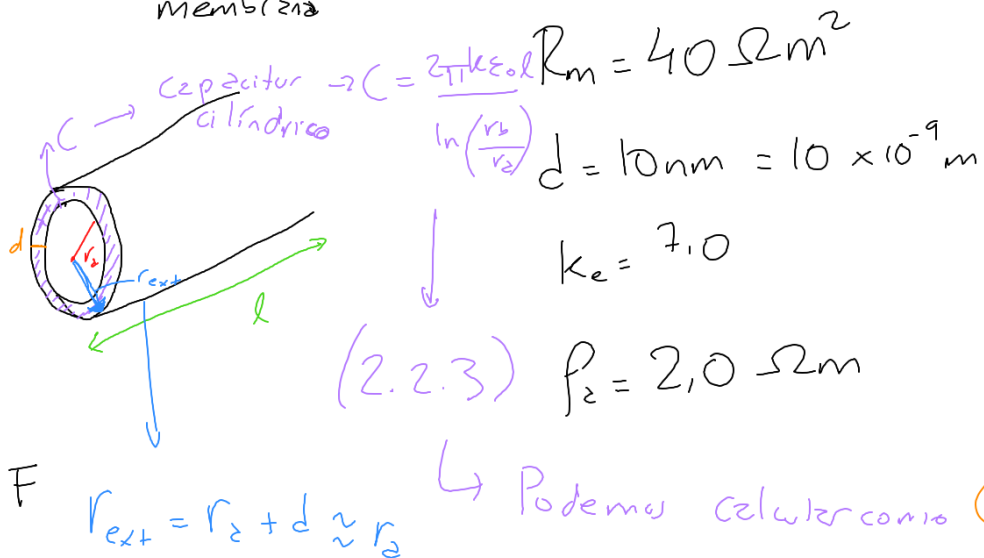

$$q(t) = q_m (1 - e^{-t/\tau})$$

$$t^* / q(t^*) = \frac{1}{2} q_m \Rightarrow$$

$$1 - e^{-t^*/\tau} = \frac{1}{2} \Rightarrow t^* = -\tau \log(1 - 1/2)$$

$t^* = 2.15 \text{ s}$

$$t^{**} / q(t^{**}) = 0.99 q_m \Rightarrow 1 - e^{-t^{**}/\tau} = 0.99 \Rightarrow t^{**} = -\tau \log(1 - 0.99)$$

$t^{**} = 14.3 \text{ s}$